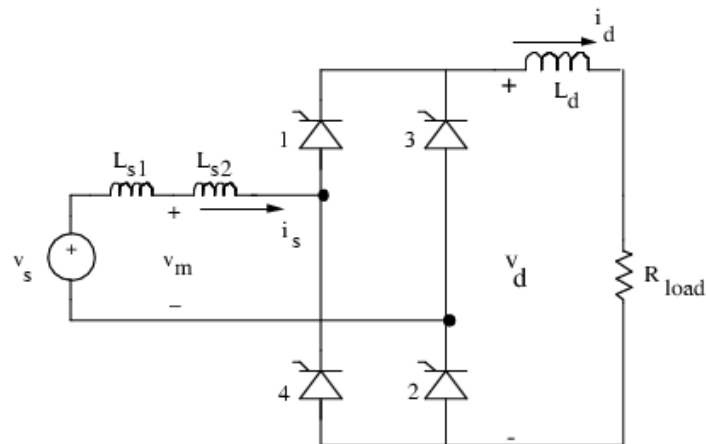


LAB 02 - THYRISTOR RECTIFIER BRIDGE



Nominal values: $V_s(\text{rms}) = 120 \text{ V}$ at 60 Hz
 $L_{s1} = 0.2 \text{ mH}$
 $L_{s2} = 1.0 \text{ mH}$
 $L_d = 20 \text{ mH}$
 $R_{\text{load}} = 5 \Omega$
 delay angle $\alpha = 45^\circ$

1.
 - (a) Obtain v_s , v_d and i_d waveforms.
 - (b) Obtain v_s and i_s waveforms.
 - (c) Obtain v_m and i_s waveforms.

2. Replace R_{load} and L_d by a DC current source I_d equal to average value of i_d . Make $L_{s1}=L_{s2}=0$

 By means of Fourier analysis of i_s , calculate $I_{s\text{RMS}}$, the first harmonic component $I_{s1\text{RMS}}$, %THD in the input current, the input displacement power factor (DSP) and the input power factor PF. Compare with the theoretical values.

3. Make $L_{s1}=0.2\text{mH}$ and $L_{s2}=1.0 \text{ mH}$. From the plots, obtain the commutation interval u . Compare with the theoretical value.

4. Verify that average DC value V_d is given by

$$V_d = 0.9 V_s \cos \alpha - \frac{2\omega L_s}{\pi} I_d.$$

5. Make delay angle $\alpha=135^\circ$. Verify that average DC value V_d is now negative