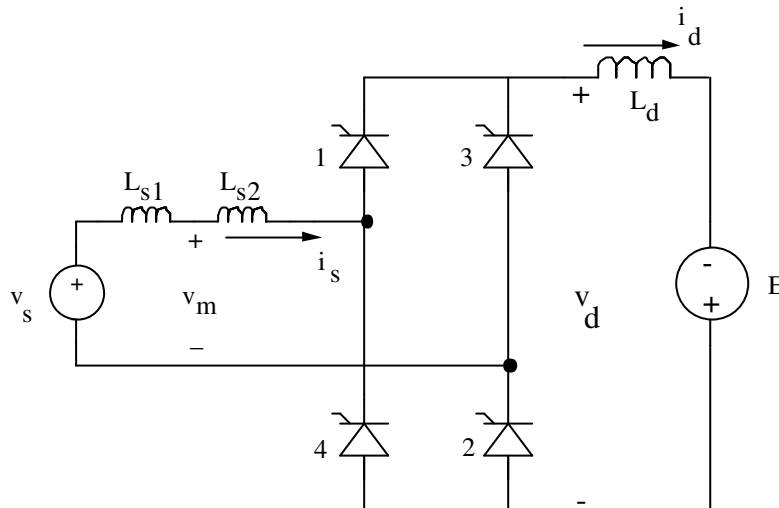


EXAMPLE 4

1-Phase Thyristor Inverter



Nominal Values: $V_s(\text{rms}) = 120 \text{ V}$ at 60 Hz
 $L_{s1} = 0.2 \text{ mH}$
 $L_{s2} = 1.0 \text{ mH}$
 $L_d = 20 \text{ mH}$
 $E = 88 \text{ V (dc)}$
 delay angle $\alpha = 135^\circ$

Problems

- Obtain v_s , v_d and i_d waveforms using Thyinv1.
 - Obtain v_s and i_s waveforms.
- Calculate I_s , %THD in the input current, the input displacement power factor and the input power factor.
- Study the startup of inverter operation. Increase the delay angle to a value close to 180° (for example, 150°) and look at the v_s , v_d and i_d waveforms. Repeat the above procedure by reducing α slowly to its nominal value of 135° . Plot the average dc current I_d versus α .

Reference: Section 6-3-4, pages 135 - 138.

PSpice Schematic: Thyinv1

[Copyright © 2003, Adapted with permission from "Power Electronics Modeling Simplified using PSpice™ (Release 9)": <http://www.mnpere.com>]