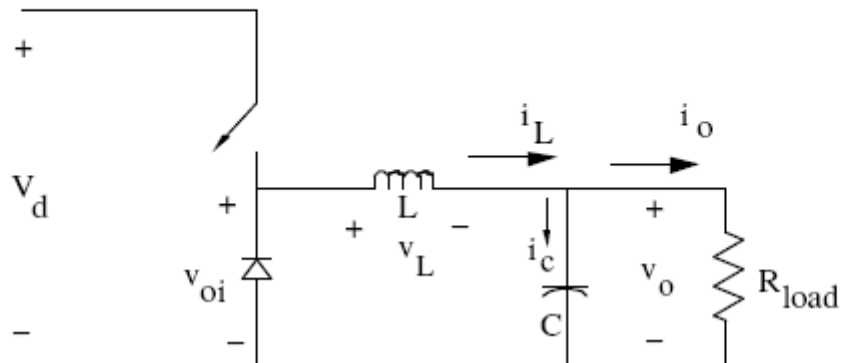


LAB 04

Step-down (BUCK) dc-dc Converter



Nominal Values:

- $V_d = 8 \text{ V (dc)}$
- $L = 5 \mu\text{H}$
- $r_L = 10 \text{ m}\Omega$
- $C = 100 \mu\text{F}$
- $R_{\text{load}} = 0.5 \Omega$
- $f_s = 100 \text{ kHz}$
- switch duty ratio $D = 0.75$

1.

In steady state, obtain the following waveforms using Buckconv:

- (a) v_L and i_L waveforms.
- (b) v_o , i_L and i_c waveforms

2.

Increase the load resistance to 10Ω . Obtain v_L and i_L waveforms in the discontinuous conduction mode [Hint: use $V(0) = 5.8\text{V}$ and $I_L(0) = 0$]. Check if the results agree with the following equation:

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + \frac{1}{4} \left(\frac{I_o}{I_{LB,\text{max}}} \right)}$$

where $I_{LB,\text{max}} = \frac{V_d}{8Lf_s}$.

Theoretically, what is the D value which would return V_o to the nominal 6 Volt value? Confirm in SPICE.

Go back to continuous mode (load resistance 0.5Ω)

3. Obtain the peak-to-peak ripple in the output voltage and check to see if results agree with the analytical calculations.

4. Calculate the rms value of the current through the output capacitor as a ratio of the average load current I_o