

$$R_D = \frac{(+5 - 1)V}{0.4 \text{ mA}} = 10 \text{ k}\Omega$$

em saturação:

$$I_D = \frac{1}{2} \mu_N C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$


$$0.4 \text{ mA} = \frac{1}{2} \cdot 20 \cdot 10^{-6} \cdot \frac{400}{10} (V_{GS} - 2)^2$$

$$V_{GS} = 3 \text{ V} \quad (V_{GS} = 1 \text{ V} \Rightarrow V_{GS} < V_T !)$$

↓

$$V_S = -3 \text{ V}$$
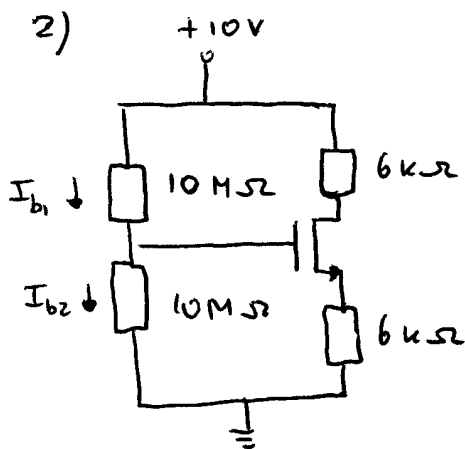
$$R_S = \frac{-3 - (-5) \text{ V}}{0.4 \text{ mA}} = 5 \text{ k}\Omega$$



$$V_G = \frac{10 \text{ M}}{10 \text{ M} + 10 \text{ M}} \times 10 \text{ V} = 5 \text{ V}$$

$$I_{b1} = I_{b2} = \frac{10 - 5 \text{ V}}{10 \text{ M}\Omega} = 5 \mu\text{A}$$

Vamos assumir que o transistor está a funcionar na zona de saturação

$$I_D = \frac{1}{2} \mu_N C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_D = 0.5 \cdot 10^{-3} (5 - 6 \cdot 10^3 I_D - 1)^2$$

Soluções: $I_D = 0.89 \text{ mA}$ $I_D = 0.5 \text{ mA}$

$$V_S = 5.34 \text{ V}$$

$$V_G = 5 \text{ V}$$

$$V_{GS} < V_T !$$

erro!

$$V_S = 3 \text{ V}$$

$$V_D = 7 \text{ V}$$

$$V_{DS} = 4 \text{ V}$$

$$V_{GS} = 2 \text{ V}$$

$$V_{DS} > V_{GS} - V_T \Rightarrow \text{zona de}$$

$$V_G = 5 \text{ V}$$


$$V_S = 6 \cdot 10^3 I_D$$

$$V_D = 10 - 6 \cdot 10^3 I_D$$

$$\frac{1}{2} \mu_N C_{ox} \frac{W}{L} = 0.5 \cdot 10^{-3}$$

$$V_T = 1 \text{ V}$$

3)

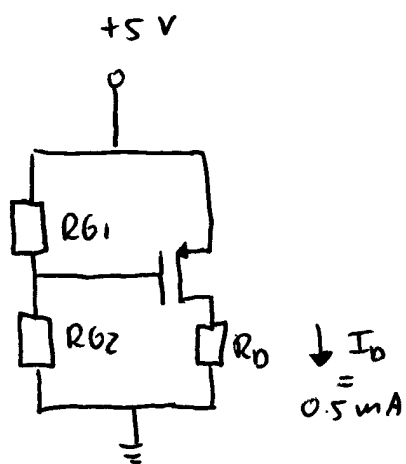

$$R_D = \frac{V_D}{I_D} = \frac{3V}{0.5mA} = 6 k\Omega$$

saturação $V_{SD} > V_{SG} + |V_T|$

$$V_G > +2V$$

Em saturação:


$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_T|)^2$$

$$0.5 \cdot 10^{-3} = \frac{1}{2} \cdot 10^{-3} (5 - V_G - 1)^2$$

$$\Rightarrow V_G = 3V \Rightarrow R_{G2} = \frac{3}{2} R_{G1}$$

(ex. $R_{G1} = 2 M\Omega, R_{G2} = 3 M\Omega$)

R_D máxima (com saturação)

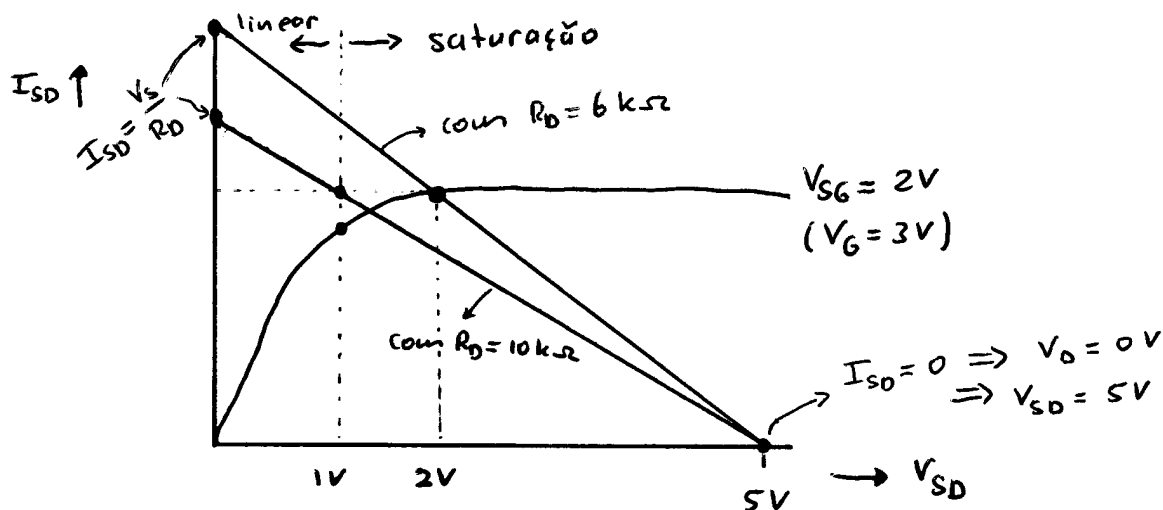

saturação: $V_{SD} \geq V_{SG} - |V_T|$

$$V_{SD} \geq 2 - 1 = 1$$

$$V_D \leq 4V \Rightarrow R_D \leq \frac{4V}{0.4mA} = 10 k\Omega$$

NB: I_D independente de V_{SD} (saturação)