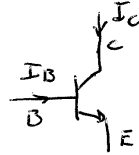


ELECTRÓNICA 1 - AULA 9

TRANSISTORES BJT. MODELOS DE PEQUENO SINAL. CONFIGURAÇÕES BÁSICAS. EMISSOR COMUM. COLECTOR COMUM. BASE COMUM.

Modelos de pequeno sinal


$$I_B = I_S e^{V_{BE}/V_T} \left(1 + \frac{1}{V_E} V_{CE}\right)$$



com $V_T = \frac{kBT}{q} \approx 25 \text{ mV}$

$$I_C = \beta I_B = \beta I_S e^{V_{BE}/V_T} \left(1 + \frac{1}{V_E} V_{CE}\right)$$


modelos π

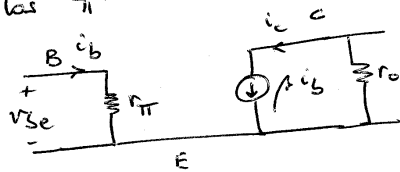

$$A_I = \frac{\partial I_C}{\partial I_B} = \beta$$

$$\frac{1}{r_{\pi}} = \frac{\partial I_B}{\partial V_{BE}} \bigg|_{V_{CE} = V_{CEQ}} = \frac{1}{V_T} I_S e^{V_{BE}/V_T} = \frac{I_B}{V_T} = \frac{1}{\beta} \frac{I_C}{V_T}$$


$$r_{\pi} = \beta \frac{V_T}{I_C}$$

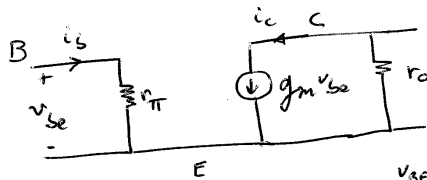

$$g_m = \frac{\partial I_C}{\partial V_{BE}} \bigg|_{V_{CE} = V_{CEQ}} = \frac{1}{V_T} \beta I_S e^{V_{BE}/V_T} = \frac{I_C}{V_T}$$

$$\frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}} \approx \frac{I_C}{V_E}$$

modelo T

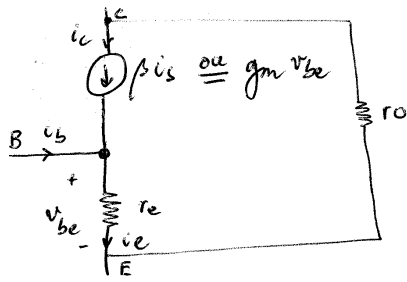

$$\frac{1}{r_e} = \left. \frac{\partial I_E}{\partial v_{BE}} \right|_{v_{BE} = v_{BE\phi}}$$


$$\frac{1}{r_e} = \frac{1}{V_T} (\beta+1) I_E e^{v_{BE}/V_T}$$

$$\frac{1}{r_e} = \frac{I_E}{V_T} = \frac{\beta+1}{\beta} \frac{I_C}{V_T}$$

notar que $r_e = \frac{1}{\beta+1} r_{\pi}$

notar que $g_m = \frac{\beta}{r_{\pi}} \approx \frac{1}{r_e}$


CONFIGURAÇÃO DE EMISSOR COMUM

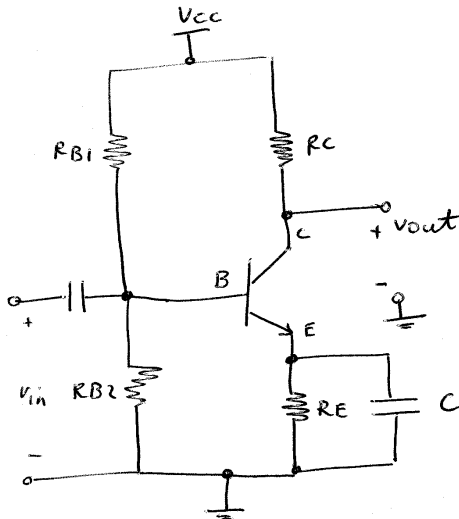

modelo de pequeno sinal


- a) com condensador C
tal que $|Z_C| = \frac{1}{2\pi f C} \approx 0$

a) Com condensador

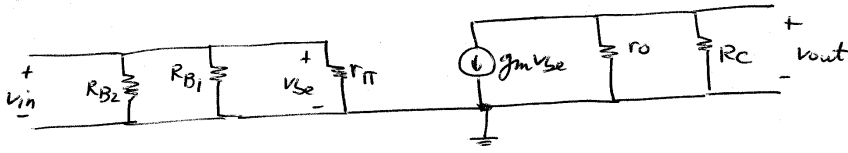

$$A_V = \frac{v_{out}}{v_{in}} = \frac{-g_m v_{be} (r_o \parallel R_C)}{v_{be}} = -g_m (r_o \parallel R_C) \approx -g_m R_C$$

b) sem condensador e ignorando r_o

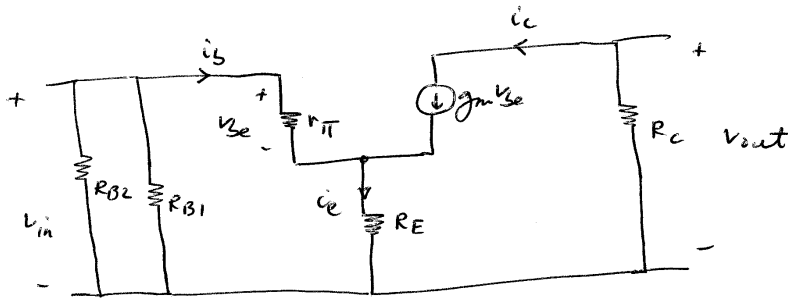

$$v_{out} = -R_C g_m v_{be}$$

$$v_{in} = v_{be} + R_E i_e$$

$$\text{mas } i_e = i_b + i_c = \frac{v_{be}}{r_{\pi}} + g_m v_{be}$$

$$\text{logo } v_{in} = v_{be} + R_E \left(\frac{1}{r_{\pi}} + g_m \right) v_{be}$$

$$v_{in} = \left(1 + \frac{R_E}{r_{\pi}} + g_m R_E \right) v_{be}$$

$$\text{logo } A_V = \frac{v_{out}}{v_{in}} = - \frac{R_C g_m}{1 + \frac{R_E}{r_{\pi}} + g_m R_E} \approx - \frac{R_C}{R_E}$$

Resistência de entrada


$$R_{in} = \frac{v_{in}}{i_{in}}$$

a) com condensador

$$R_{in} = R_{B2} \parallel R_{B1} \parallel r_{\pi} \approx r_{\pi}$$

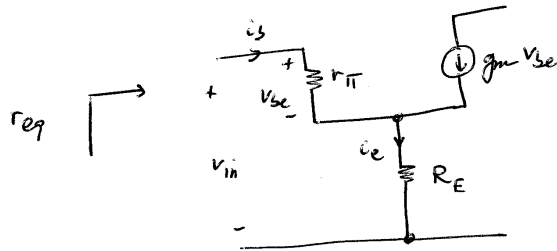b) sem condensador

$$R_{in} = R_{B2} \parallel R_{B1} \parallel r_{eq}$$




$$r_{eq} = \frac{v_{in}}{i_b} = \frac{v_{be} + R_E i_e}{i_b} = \frac{r_{\pi} i_b + R_E (g_m r_{\pi} i_b + i_b)}{i_b}$$

$$r_{eq} = r_{\pi} + R_E g_m r_{\pi} + R_E = r_{\pi} + (1 + g_m r_{\pi}) R_E$$

Resistência de saída


$$R_{out} = \frac{v_{out}}{i_{out}} = r_o \parallel R_C \approx R_C$$

CONFIGURAÇÃO DE COLECTOR COMUM

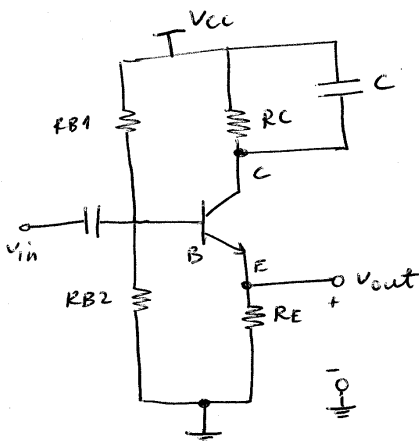


modelo de pequeno sinal

a) com condensador C

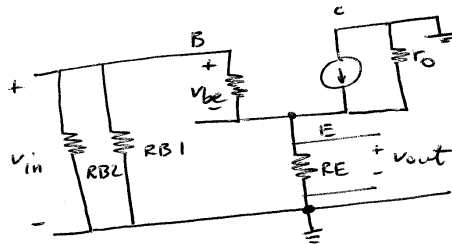

circuito equivalente

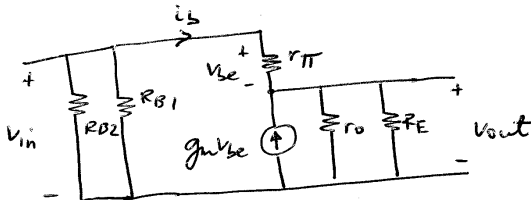

$$v_{out} = (r_o \parallel R_E) (g_m v_{be} + i_b)$$

$$v_{out} = (r_o \parallel R_E) \left(g_m v_{be} + \frac{v_{be}}{r_{\pi}} \right)$$

$$v_{out} = (r_o \parallel R_E) \left(g_m + \frac{1}{r_{\pi}} \right) v_{be}$$

mas $v_{in} = v_{be} + v_{out}$ logo $v_{be} = v_{in} - v_{out}$

substituindo

$$v_{out} = (r_o \parallel R_E) \left(g_m + \frac{1}{r_{\pi}} \right) (v_{in} - v_{out})$$

$$A_V = \frac{(r_o \parallel R_E) \left(g_m + \frac{1}{r_{\pi}} \right)}{1 + (r_o \parallel R_E) \left(g_m + \frac{1}{r_{\pi}} \right)}$$


mas $r_{\pi} = \frac{v_T}{I_B}$

$$g_m = \frac{I_C}{v_T} = \beta \frac{I_B}{v_T} = \frac{\beta}{r_{\pi}}$$

logo $A_V \approx \frac{g_m R_E}{1 + g_m R_E} \approx 1$ (mas menor que 1)

resistência de entrada
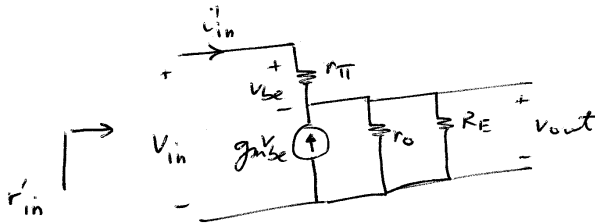
$$R_{in} = \frac{v_{in}}{i_{in}} = R_{B1} \parallel R_{B2} \parallel r'_{in}$$




$$\begin{aligned} v_{in} &= v_{be} + v_{out} \\ &= r_{\pi} i_{in} + (g_m v_{be} + i_{in}) (r_o \parallel R_E) \\ &= r_{\pi} i_{in} + (g_m r_{\pi} i_{in} + i_{in}) (r_o \parallel R_E) \end{aligned}$$

$$r'_{in} = \frac{v_{in}}{i_{in}} = r_{\pi} + (1 + g_m r_{\pi}) (r_o \parallel R_E)$$

$$r'_{in} \approx (g_m R_E) r_{\pi}$$

resistência de saída

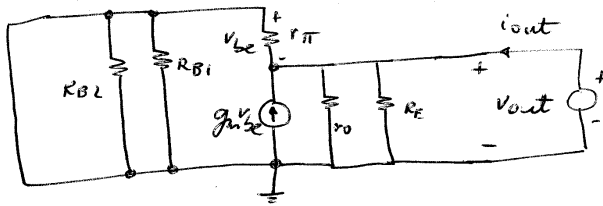

$$R_{out} = \frac{v_{out}}{i_{out}} = \left(\frac{1}{g_m} \parallel r_{\pi} \parallel r_o \parallel R_E \right)$$

$$R_{out} \approx \frac{1}{g_m}$$