

# Exam Electronics II

(1)


II / VIII / 2011

## Question 1

a)  $A = \infty \Rightarrow V_p = V_n$  or saturation  
 $r_i = \infty, r_o = 0$


b)

- $I_p = 0$  (because  $r_i = \infty$ )

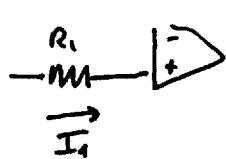

- Therefore  $I_i = 0$
- That means  $V_p = V_i - I_i R_i = V_i$
- That means  $V_n = V_i$  (rule + above)

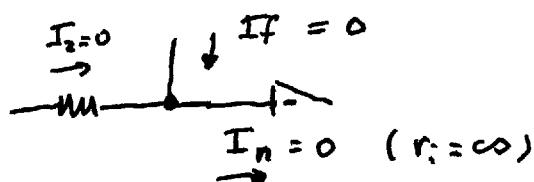
- If  $V_n = V_i$  then  $R_2$  has no current. That means that  $I_f$  is zero (using Kirchoff Law)



- If  $I_f = 0$  then  $\Delta V_f = 0 \Rightarrow V_o = V_n - I_f R_f = V_i$   
 $\Rightarrow V_o = V_i$


## Question 2

common mode gain

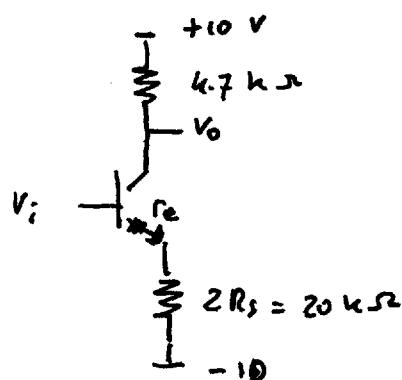

$$A_V^{CM} = \frac{4.7 \text{ k}\Omega}{20 \text{ k}\Omega + 53.8 \text{ }\mu\Omega} \left( \frac{R_c}{2R_g + R_e} \right)$$

$$= -0.234$$

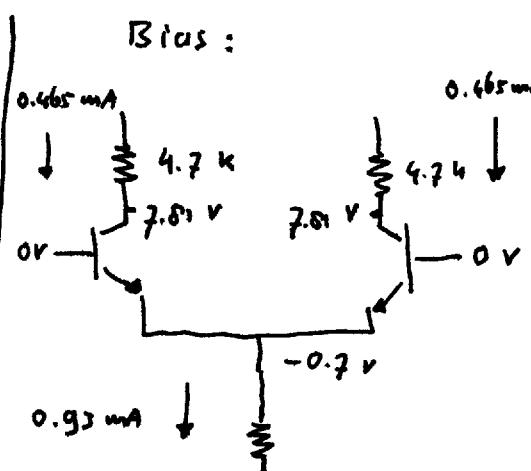


$$r_e = \frac{25 \text{ mV}}{0.465 \text{ mA}} = 53.8 \text{ }\mu\Omega$$

$$r_o = \frac{1000 \text{ V}}{0.465 \text{ mA}} = 2.1 \text{ M}\Omega$$

$$d \approx 1, I_c = I_E$$

Differential mode gain

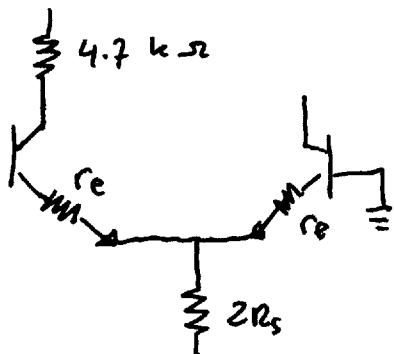


$$A_v^{\text{Dm}} = + \frac{R_c}{r_e + r_e \parallel 2R_s} \approx$$

$$\approx + \frac{R_c}{2r_e} = + 43.68$$


$$\text{CMRR} = \left| \frac{A_v^{\text{dm}}}{A_v^{\text{cm}}} \right| = \frac{43.68}{0.234} = 187$$

Question 3

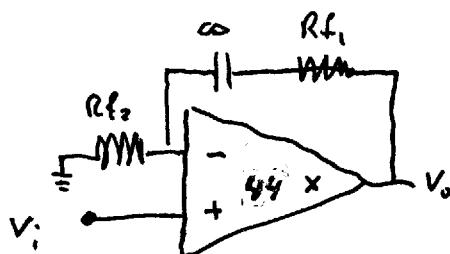


The circuit is equal to the opamp circuit

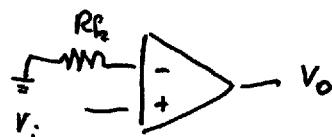For OC the  $\frac{1}{f}$  is open circuit and we get our  
44 × amplifier back



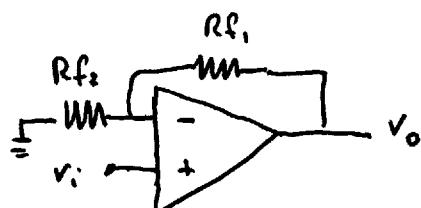For any other frequency  $\frac{1}{f}$  is a short circuit and the circuit becomes




$$\beta = - \frac{R_f_2}{R_f_1 + R_f_2} = -0.5$$

$$\frac{V_o}{V_i} = \frac{A}{1 - A\beta} = \frac{187}{1 + 187 \times 0.5} = 1.98$$

## Question 4


\* Common mode: The feedback capacitor  $C_{cc}$  has no effect!! Since both sides of the capacitor always have the same voltage (because of symmetry) the charge in the capacitor is zero:  $Q = C \cdot \Delta V = 0$ . If  $Q = 0$ ,  $I = \frac{dQ}{dt} = 0$ , always and the capacitor might as well not have been there at all.

We get the following circuit in CM:

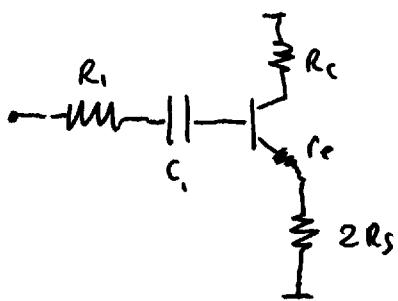

$C_i$  is part of a high-pass filter (HPF).

The equivalent resistance is given by

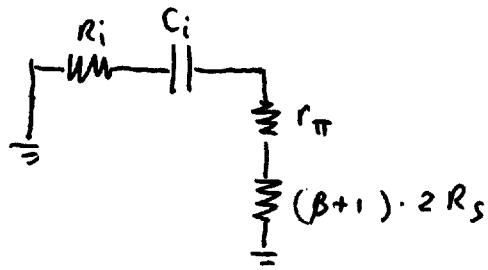


$$\begin{aligned} R_{eff} &= R_i + r_{\pi} + (\beta+1) \cdot 2R_s \\ &= 1 \text{ k}\Omega + (400) \cdot (20 \text{ k}\Omega + 53.8 \Omega) \\ &= 2.0 \text{ M}\Omega \end{aligned}$$


$$\tau_L = R_{eff} \cdot C_i = 2 \text{ M}\Omega \cdot 1 \text{ pF} = 2 \text{ s}$$

$$f_L = \frac{1}{2\pi\tau_L} = 80 \text{ mHz}$$

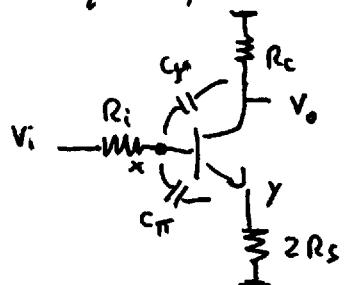\* High frequency CM: The capacitor  $C_i$  is short circuit.



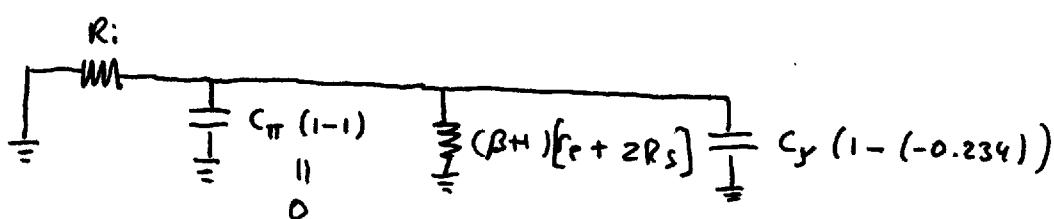The gain between  $V_x$  and  $V_o$  is  $-0.234$  (for Miller effect). The gain between  $V_x$  and  $V_y \approx 1$ . We get at the entrance the following equivalent circuit:



(4)

$$C_{\text{eff}} = C_T \cancel{\left(1 - \frac{1}{\beta+1}\right)} + C_r \left(1 - \left(1 - 0.234\right)\right)$$

$$= 12.34 \text{ pF}$$


$$R_{\text{eff}} = R_i \parallel (\beta+1)[r_e + 2R_s]$$

$$= 1k\Omega \parallel 2M\Omega \approx 1k\Omega$$

$$\tau_{H1} = R_{\text{eff}} \times C_{\text{eff}} = 12.34 \text{ ns}$$

$$f_{H1} = \frac{1}{2\pi\tau_{H1}} = 12.9 \text{ MHz}$$

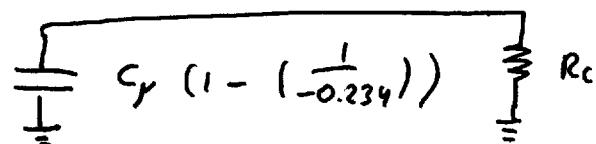At the exit we get following equivalent circuit:



$$C_{\text{eff}} = C_r \left(1 - \left(\frac{1}{-0.234}\right)\right) = 52.7 \text{ pF}$$

$$R_{\text{eff}} = R_C = 4.7 k\Omega$$




$$\tau_{H2} = R_{\text{eff}} \times C_{\text{eff}} = 2.48 \times 10^{-7} \text{ s}$$

$$f_{H2} = \frac{1}{2\pi\tau_{H2}} = 642 \text{ kHz}$$

$$\tau_{\text{total}} = \tau_{H1} + \tau_{H2} = 2.60 \times 10^{-7} \text{ s}$$

$$f_{H\text{total}} = \frac{1}{2\pi\tau_{\text{total}}} = 611 \text{ kHz}$$

$$\log \left| \frac{V_o}{V_i} \right|$$

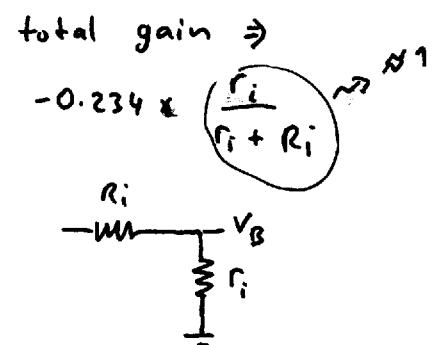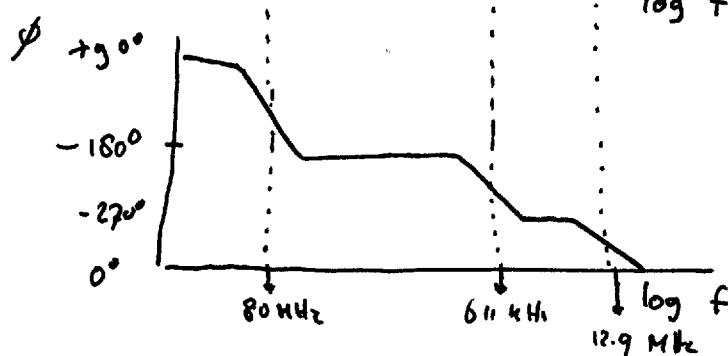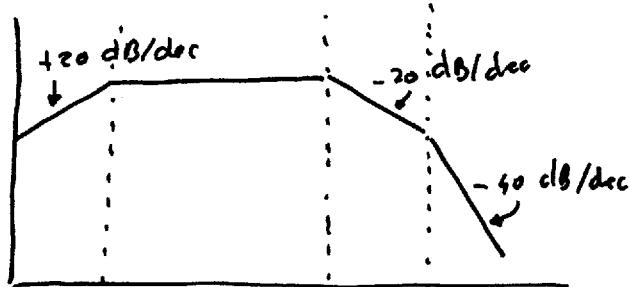

$$R_i = 2 M\Omega = (\beta+1)[r_e + 2R_s]$$


$$A_v = -0.234$$

(5)

\* Differential mode : low frequencies

The two  $C_i$ 's are HPF. We will use the short-circuit time constants idea to find the two  $\tau$ 's :

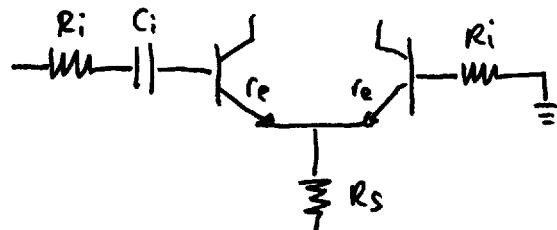Left side : ( $C_i$  right is short circuit) :




$$\begin{aligned} R_{eff} &= R_i + (\beta + 1) \left[ r_e + R_s / (r_e + \frac{R_i}{\beta + 1}) \right] \\ &\approx 2R_i + 2(\beta + 1)r_e \\ &= 2k\Omega + 107.6 \Omega \end{aligned}$$


$$\tau_L = R_{eff} \times C_i = 2.1 \text{ k}\Omega \times 10 \mu\text{F} = 2.1 \text{ ms}$$

$$f_L = 75.5 \text{ Hz}$$

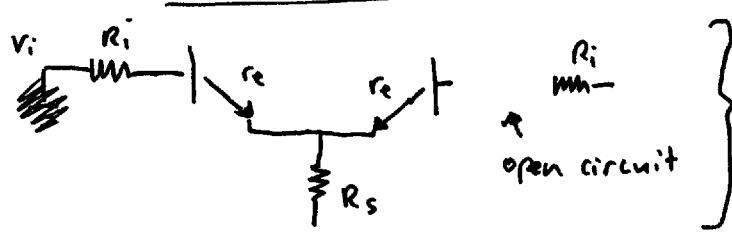
Right side : ( $C_i$  left is short circuit) : This is also a HPF because :



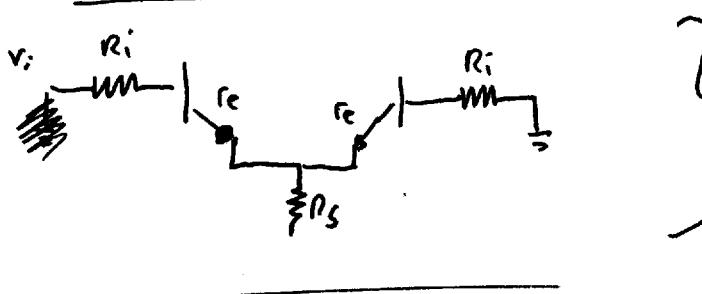low frequencies  
 $A_v \approx \frac{R_c}{R_s} \approx 0$



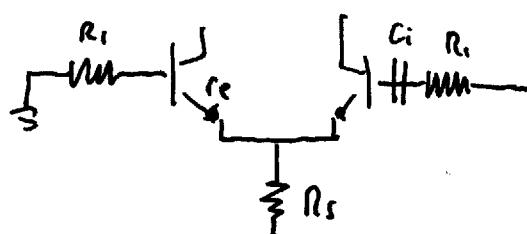High Frequencies:  
 $A_v \approx \frac{R_c}{r_e + R_s / (r_e + \frac{R_i}{\beta + 1})}$   
 $\approx \frac{R_c}{2r_e}$  is large




$R_{eff}$  is equal to  $C_i$  of left side

$$\Rightarrow \tau_L = 2.1 \text{ ms}, f_L = 75.5 \text{ Hz}$$

$$\tau_{total} = \left( \frac{1}{\tau_L} + \frac{1}{\tau_C} \right)^{-1} = 1.05 \text{ ms}, f_{Ltotal} = f_L + f_C = 151 \text{ Hz}$$

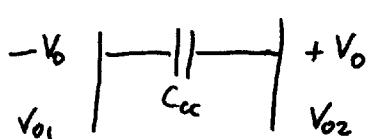
(6)

\* Differential mode : High frequencies. The  $C_i$ 's are already short circuit. The capacitor  $C_{cc}$  is also cutting at high frequencies. If the outputs  $-V_o$  and  $+V_o$  are



shorted (at high frequencies a capacitor is a short circuit), the outputs are both 0. (the only value that follows the symmetry rules  $V_{o1} = V_{o2}$  and  $V_{o1} = -V_{o2}$ )

At the relevant output we have

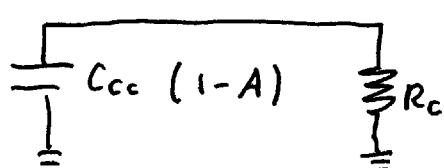

Output resistance  $r_o$  of transistor can be ignored.

$A$  is the gain between  $V_{o2} \rightarrow V_{o1}$ .  $A = -1$

$$C_M = 1 nF \times (1 - (-1)) = 2 nF$$

$$R_C = R_E = 4.7 k\Omega$$


$$\tau_{cc} = R_E \times C_M = 9.4 \text{ } \mu\text{s}$$

$$f_{cc} = 16.9 \text{ } \text{kHz}$$

The other time constants can be found as before

Note: due to our way of calculating, using open-circuit time constants, ( $C_{cc}$  is now absent):

At the entrance :

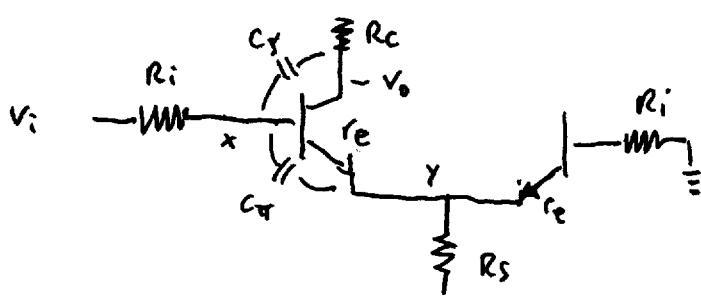

The gain between  $V_x$  and  $V_o$  is -44 (Question 2). For Miller effect of  $C_y$


The gain between  $V_x$  and  $V_y$  ~

$$\left\{ r_{in} \approx 2r_T, r_{in} = (\beta + 1) \left[ r_E + R_S // (r_E + \frac{R_1}{\beta + 1}) \right] \right\}$$

$$\frac{2 \frac{r_T}{r_E + 2r_T}}{R_i + 2r_T} = 0.91$$

(7)

We get the following equivalent circuit

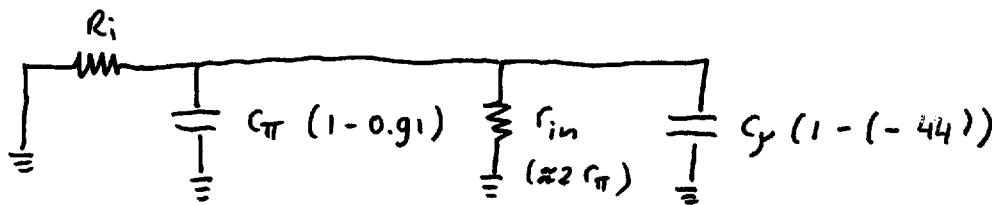


$$\begin{aligned} C_{\text{eff}} &= C_{\pi} (1 - 0.g_1) + C_y (1 - (-44)) \\ &= 10 \text{ pF} \times 0.09 + 10 \text{ pF} \times 45 = 0.45 \text{ nF} \end{aligned}$$

$$\begin{aligned} R_{\text{eff}} &= R_i // r_{\text{in}} \\ &= 1 \text{ k}\Omega // 10.7 \text{ k}\Omega = 0.91 \text{ k}\Omega \end{aligned}$$

$$\tau_{\text{in}} = C_{\text{eff}} \times R_{\text{eff}} = 0.41 \mu\text{s}$$

$$f_{\text{in}} = \frac{1}{2\pi\tau_{\text{in}}} = 389 \text{ kHz}$$

At the exit :

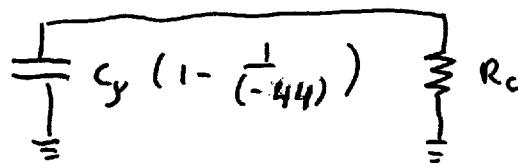

$$\tau_{\text{out}} = 10 \text{ pF} \times \left(1 + \frac{1}{44}\right) \times 4.7 \text{ k}\Omega = 48 \text{ ns}$$

$$f_{\text{out}} = \frac{1}{2\pi\tau_{\text{out}}} = 3.3 \text{ MHz}$$

$$\tau_{\text{total}} = \tau_{\text{cc}} + \tau_{\text{in}} + \tau_{\text{out}} = 9.4 \mu\text{s} + 0.41 \mu\text{s} + 48 \text{ ns} = 9.7 \mu\text{s}$$


$$f_{\text{total}} = \frac{1}{2\pi\tau_{\text{total}}} = 16.1 \text{ kHz}$$

Bandwidth: 151 Hz - 16.1 kHz

NB: the mid band gain is


$$-44 \times \frac{r_{\text{in}}}{r_{\text{in}} + R_i} = -40$$
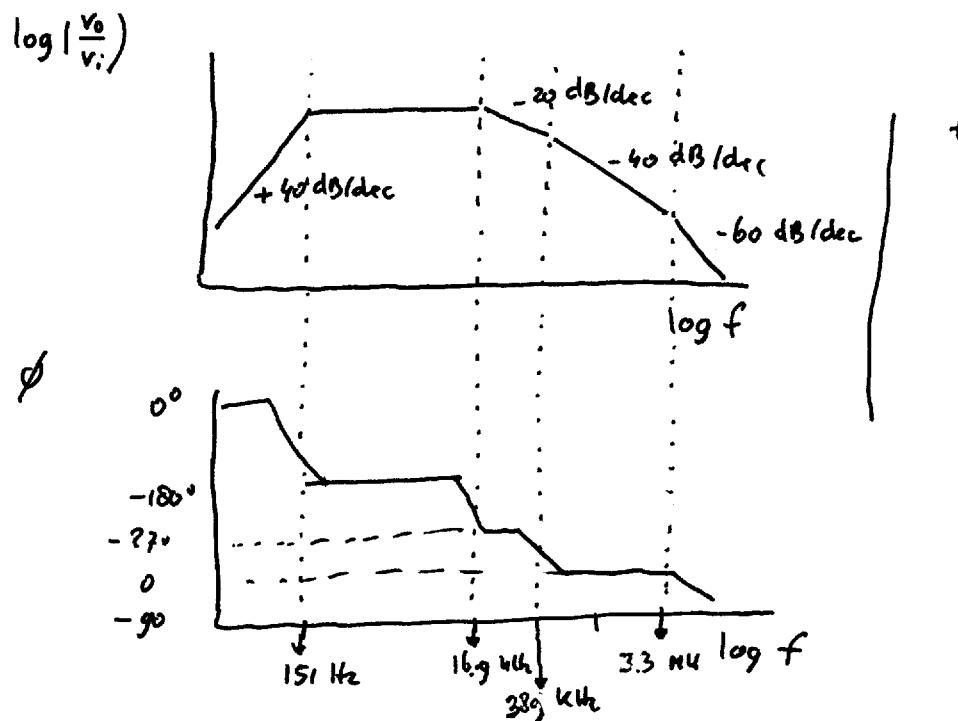
$$r_{\text{in}} = 2C_{\pi} = 10.7 \text{ k}\Omega$$



Note: the circuit was wrongly biased ( $I_B = 0$  because of  $C_i$ )


### Question 5

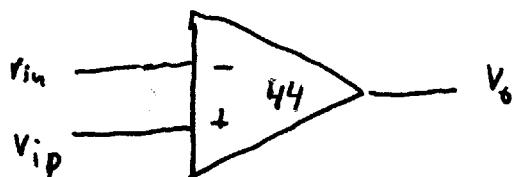


To make the circuit oscillate we have to meet the Barkhausen Criterion,  $A\beta = +1$

The A of Question 2 does not have any cut-off frequencies (poles or zeroes), and we can only use external components to have a  $\beta$  such that  $A\beta = +1$ . We can use negative feedback with 3 LPF filters (phase shift oscillator) or two capacitors and an inductor (Colpitts oscillator) or two inductors and a capacitor (Hartley oscillator) or use negative feedback with two RC networks (Wien oscillator) or both positive and negative feedback (relaxation oscillator)


(9)

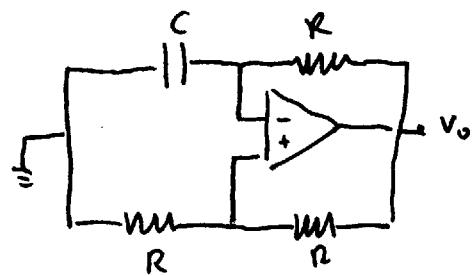


Relaxation (nur Barkhausen!)

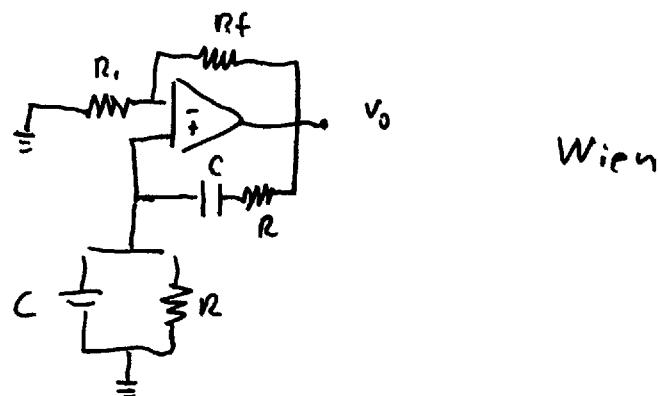


Wien

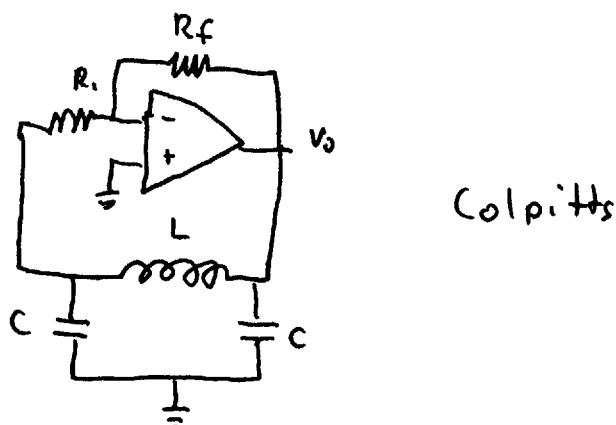

Colpitts

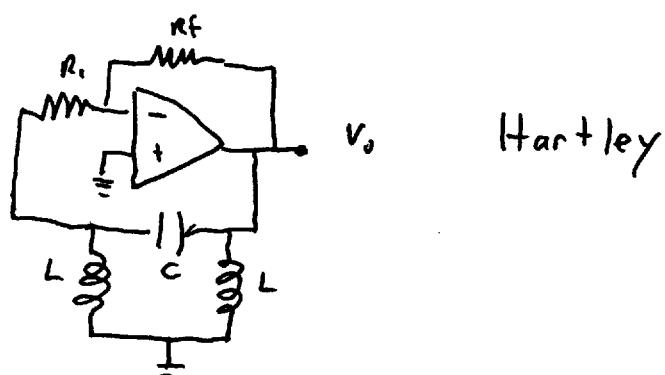


Hartley

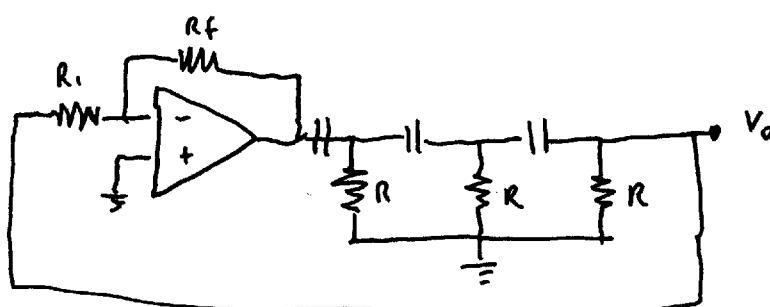

Phase Shift

Except for the first circuit, all oscillate at the frequency where  $A\beta = +1$

For instance Wien:

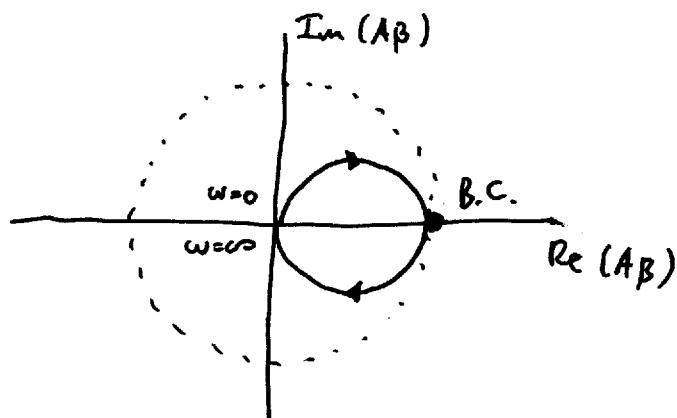


$$A\beta = A \cdot \frac{1}{3 + sRC + 1/sRC} \quad s = j\omega$$

$$\text{Im}(A\beta) = 0 \Rightarrow j(\omega RC - \frac{1}{\omega RC}) = 0$$

$$\omega = RC$$
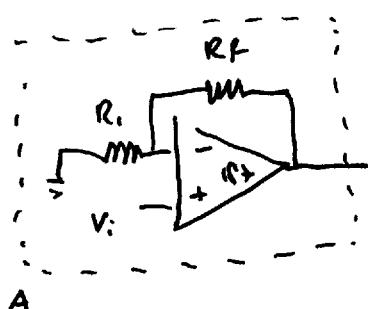
$$\text{Re}(A\beta) = \frac{A}{3} = 1 \Rightarrow A = 3$$



$$A = \frac{44}{1 + 44 \times \frac{R_1}{R_1 + R_f}}$$

A

$$\frac{R_1}{R_1 + R_f} = 0.311 \quad \text{For example } R_1 = 1k\Omega \\ R_f = 2.2 k\Omega$$

~~#~~  
end.