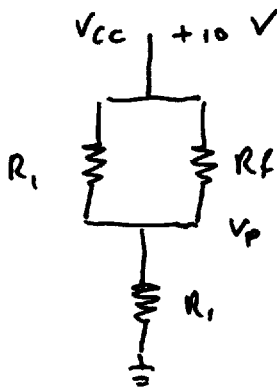


Question 1


a) See lecture notes

b) If $V_o = +V_{cc}$ we have




$$V_p = \frac{R_i}{R_i + R_i // R_f} V_{cc} = \frac{R_i + R_f}{R_i + 2R_f} V_{cc}$$

If $V_o = 0$ we have

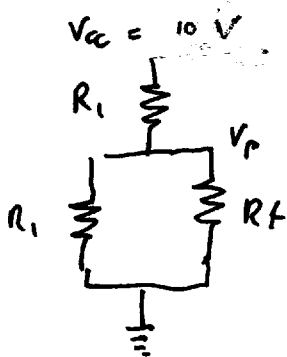

$$V_p = \frac{R_i // R_f}{R_i + R_i // R_f} V_{cc} = \frac{R_f}{R_i + 2R_f} V_{cc}$$

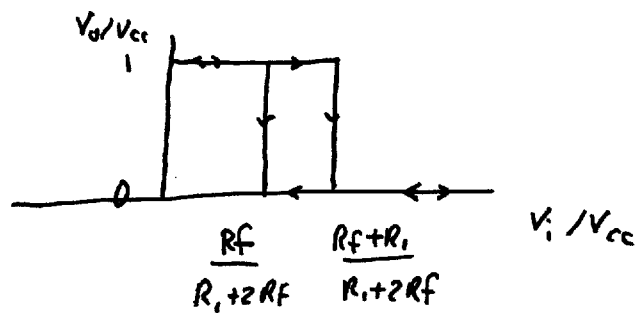

Question 2

a) $A = \infty \Rightarrow V_p = V_n$ or saturation

$r_{in} = \infty, r_{out} = 0$

$$b) V_p = \frac{R}{R + 1/j\omega C} V_i, \quad V_n = V_p = \frac{R}{R + 1/j\omega C} V_i$$

$$I_n \text{ (via } R_i) = \frac{V_i - V_n}{R_i} = \frac{V_i - \frac{R}{R + 1/j\omega C} V_i}{R_i}$$

$$V_o = V_n - I_n R_1 = \frac{R}{R + 1/j\omega C} V_i - \left(\frac{V_i - \frac{R}{R + 1/j\omega C} V_i}{R_1} \right) \times R_1$$

$$= -V_i + V_i \left(\frac{2R}{R + 1/j\omega C} \right) = V_i \times \left(\frac{R - 1/j\omega C}{R + 1/j\omega C} \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{j\omega RC - 1}{j\omega RC + 1} = \frac{(-1 + \omega^2 R^2 C^2) + j(2\omega RC)}{1 + \omega^2 R^2 C^2}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{|j\omega RC - 1|}{|j\omega RC + 1|} = \frac{\sqrt{\omega^2 R^2 C^2 + 1}}{\sqrt{\omega^2 R^2 C^2 + 1}} = 1$$




$$\phi_{V_o, V_i} = \tan^{-1} \left[\frac{\text{Im}(V_o/V_i)}{\text{Re}(V_o/V_i)} \right] = \tan^{-1} \left[\frac{2\omega RC}{(\omega RC)^2 - 1} \right]$$

$$= 180^\circ = 2 \tan^{-1}(\omega RC)$$

$$\omega = 0 \Rightarrow \tan(\phi) = -0, \phi = 180^\circ$$



$$\omega = \frac{1}{RC} \Rightarrow \tan(\phi) = \infty, \phi = +90^\circ$$

$$\omega = \infty \Rightarrow \tan(\phi) = +0, \phi = 0^\circ$$

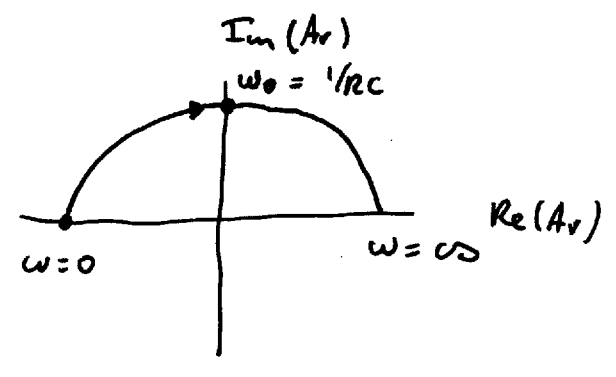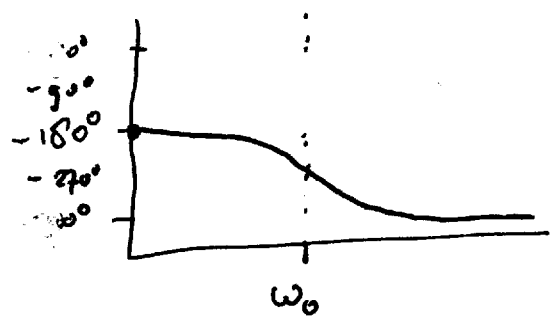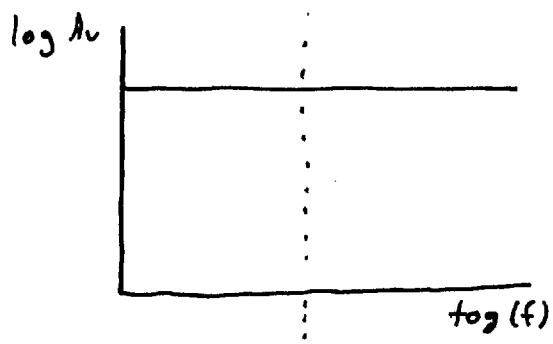

Question 3

3

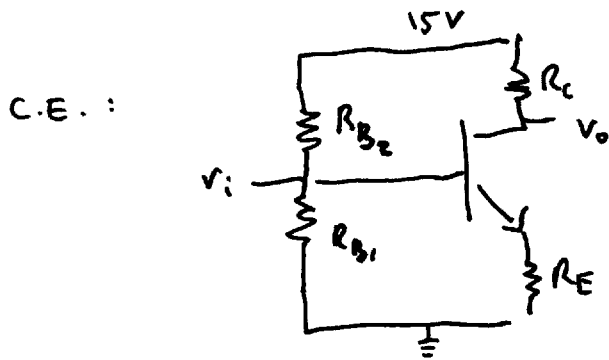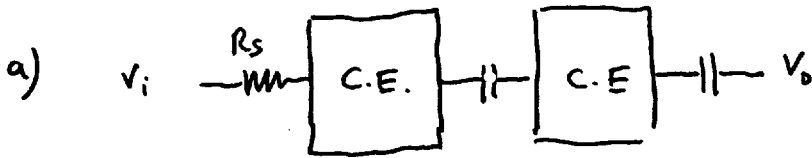

$\omega = 0 \Rightarrow$
 $\text{---|---} = \text{open circuit}$
 we have two equal, separated C.E. amplifiers

$$V_B = \frac{R_{B1}}{R_{B1} + R_{B2}} \times V_{CC} = \frac{2.2 \text{ k}\Omega}{24.2 \text{ k}\Omega} \times 15 \text{ V} = 1.36 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V} = 0.66 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{0.66 \text{ V}}{470 \Omega} = 1.41 \text{ mA}$$

$$I_C = I_E = 1.41 \text{ mA}$$

$$V_C = V_{CC} - I_C \times R_C = 15 \text{ V} - 1.41 \text{ mA} \times 4.7 \text{ k}\Omega = 8.4 \text{ V}$$


$$r_e = \frac{1}{\frac{I_E}{25 \text{ mV}}} = \frac{1}{\frac{1.41 \text{ mA}}{25 \text{ mV}}} = 17.7 \Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{200 \text{ V}}{1.41 \text{ mA}} = 142 \text{ k}\Omega$$

$r_o' \approx \infty$ (E is not grounded!)

b)
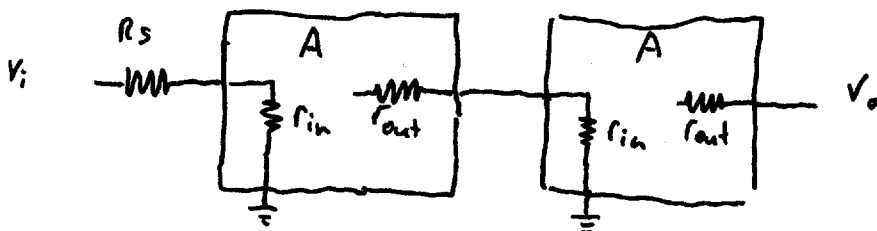
$$\text{gain} : \frac{V_o}{V_i} = - \frac{R_C}{R_E + r_e} = \frac{4.7 \text{ k}\Omega}{470 \Omega + 17.7 \Omega} = -9.64$$



$$\frac{V_o}{V_i} = \frac{r_{in}}{r_{in} + R_s} \times A \times \frac{r_{in}}{r_{out} + r_{in}} \times A$$

$$r_{out} = R_{C2} \parallel r_o' \Rightarrow \infty \approx R_{C2} = 4.7 \text{ k}\Omega$$

$$r_{in} = R_{B1} \parallel R_{B2} \parallel (\beta+1)(r_e + R_E)$$

$$= 2.2 \text{ k}\Omega \parallel 22 \text{ k}\Omega \parallel 100 (17.7 \Omega + 470 \Omega)$$

$$= 2.2 \text{ k}\Omega \parallel 22 \text{ k}\Omega \parallel 48.77 \text{ k}\Omega$$


$$= 1.92 \text{ k}\Omega$$

$$\frac{V_o}{V_i} = \frac{1.92 \text{ k}\Omega}{1.92 \text{ k}\Omega + 1 \text{ k}\Omega} \times (-9.64) \times \frac{1.92 \text{ k}\Omega}{4.7 \text{ k}\Omega + 1.92 \text{ k}\Omega} \times (-9.64)$$

$$= +17.7$$

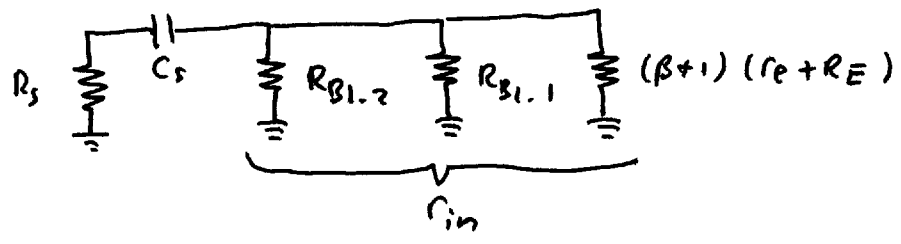c) low frequencies: C_s, C_x, C_L are HPF's

$$C_s : R_{eff} = R_s + r_{in} = 2.92 \text{ k}\Omega$$



$$\tau_s = C_s R_{eff} = 10 \mu\text{F} \times 2.92 \text{ k}\Omega = 29.2 \text{ ms}$$


$$f_s = \frac{1}{2\pi\tau_s} = 5.45 \text{ Hz}$$

$$C_x : R_{eff} = R_{C1} + r_{in} = 6.62 \text{ k}\Omega$$

$$\tau_x = C_x R_{eff} = 10 \mu\text{F} \times 6.62 \text{ k}\Omega = 66.2 \text{ ms}$$

$$f_x = \frac{1}{2\pi\tau_x} = 2.40 \text{ Hz}$$

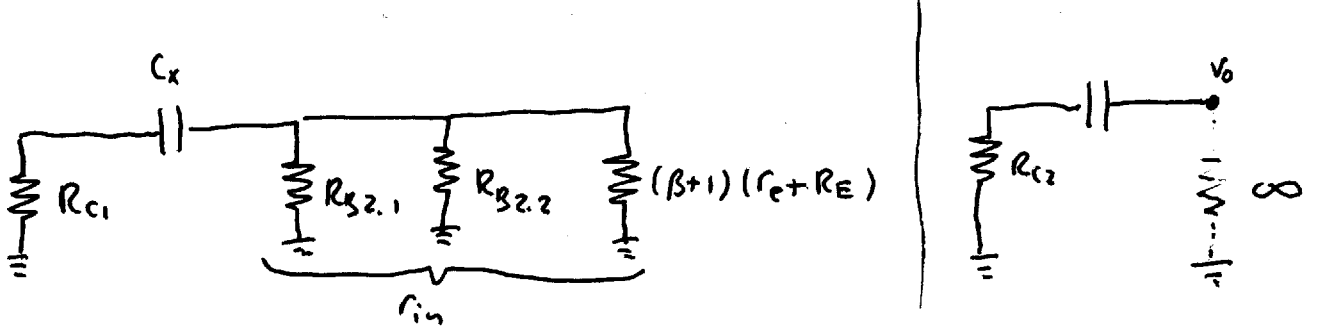
$$C_L : R_{eff} = \infty, \tau_L = \infty, f_L = 0$$



$$f_{total} = \sum_i f_i = 5.45 \text{ Hz} + 2.60 \text{ Hz} = 7.65 \text{ Hz}$$

High frequencies

• entrance C.E.1

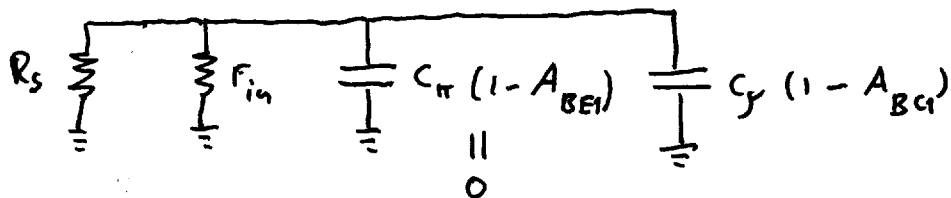

$$A_{BE1} = 1$$

$$A_{BC1} = -9.64 \times \frac{r_{in}}{r_{out} + r_{in}} = -2.80$$


$$\tau_i = (R_s \parallel r_{in}) \times C_f \times (1 - A_{BC1})$$

$$= (1 \text{ k}\Omega \parallel 1.92 \text{ k}\Omega) \times 5 \text{ pF} \times (3.80)$$

$$= 1.2 \times 10^{-8} \text{ s}$$

$$f_i = \frac{1}{2\pi\tau_i} = 12.7 \text{ MHz}$$

• between C.E.1 and C.E.2

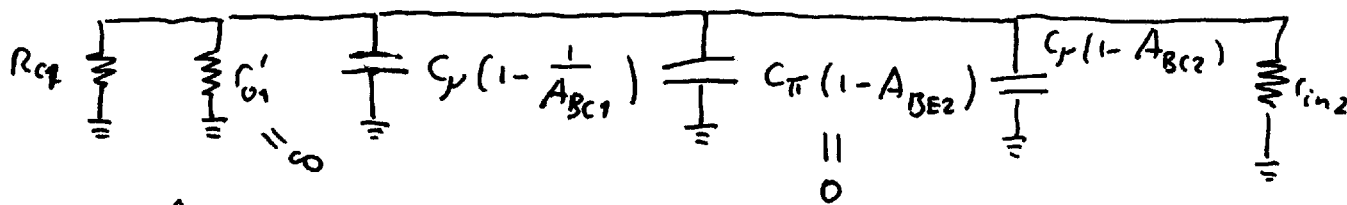

$$A_{BE2} = 1$$

$$A_{BC2} = -9.64$$

$$\tau_{12} = (R_{c1} \parallel r_{in2}) \times C_f \times \left(1 - \frac{1}{A_{BC1}} + 1 - A_{BC2}\right)$$


$$= (4.7 \text{ k}\Omega \parallel 1.92 \text{ k}\Omega) \times 5 \text{ pF} \times \left(1 + \frac{1}{2.8} + 1 + 9.64\right)$$

$$= 1.36 \text{ k}\Omega \times 60 \text{ pF}$$

$$= 81.8 \text{ ns}$$

$$f_{12} = \frac{1}{2\pi\tau} = 1.95 \text{ MHz}$$

• exit C.E.2

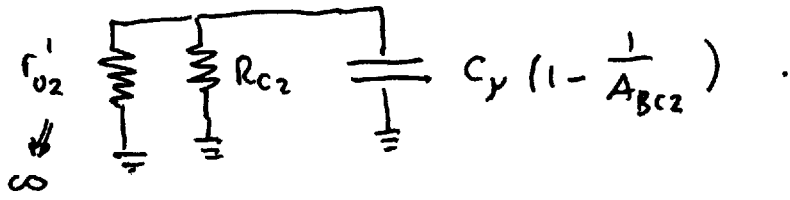

$$A_{Bc2} = -9.64$$



$$\tau_0 = R_{c2} \times C_y \times (1 - \frac{1}{A_{Bc2}})$$

$$= 4.7 \text{ k}\Omega \times 5 \text{ pF} \times (1 + \frac{1}{9.64}) =$$

$$= 2.5 \times 10^{-8} \text{ s}$$



$$f_0 = \frac{1}{2\pi \tau_0} = 6.13 \text{ MHz}$$

$$\begin{aligned} \tau_{total} &= \sum \tau_i = \tau_c + \tau_{i2} + \tau_0 \\ &= 119 \text{ ns} \\ f_{total} &= 1.34 \text{ MHz} \end{aligned}$$

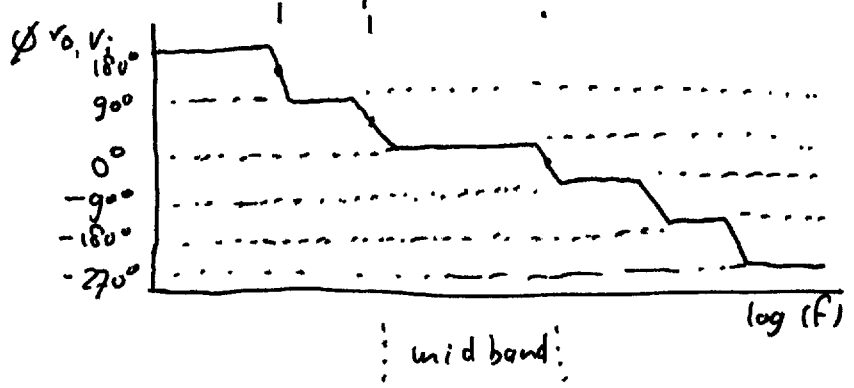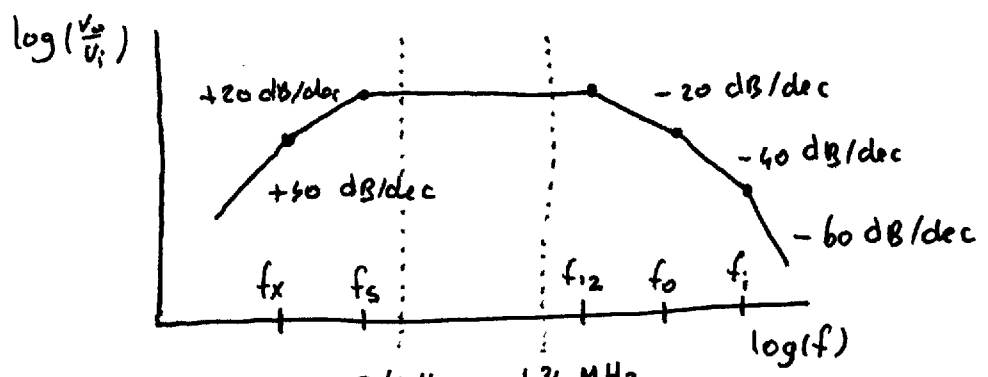

Question 4

7

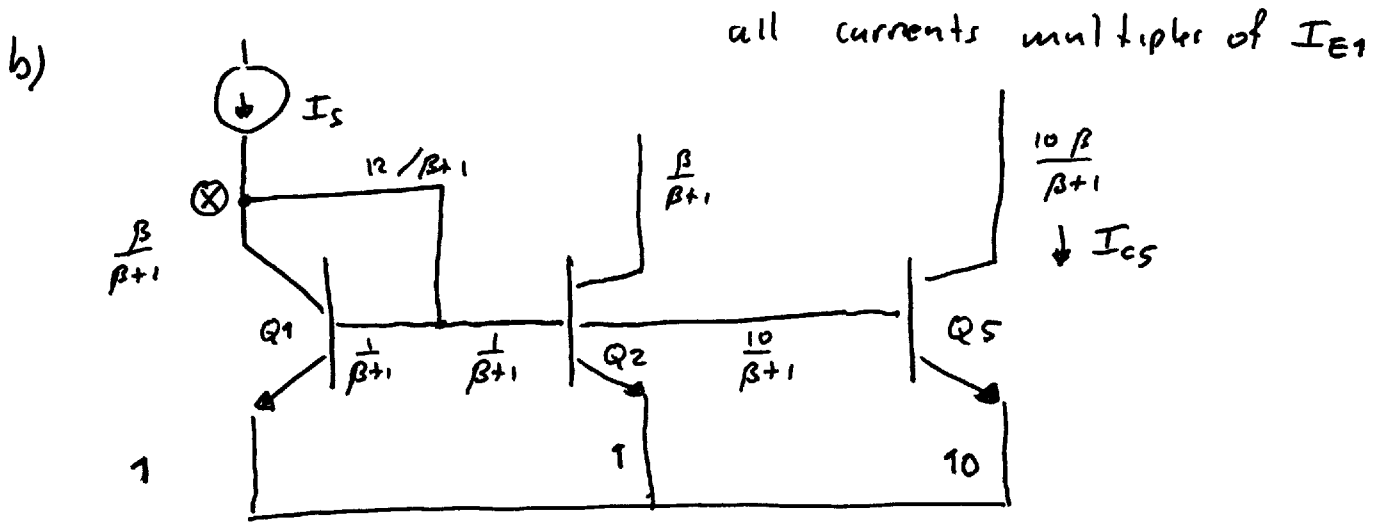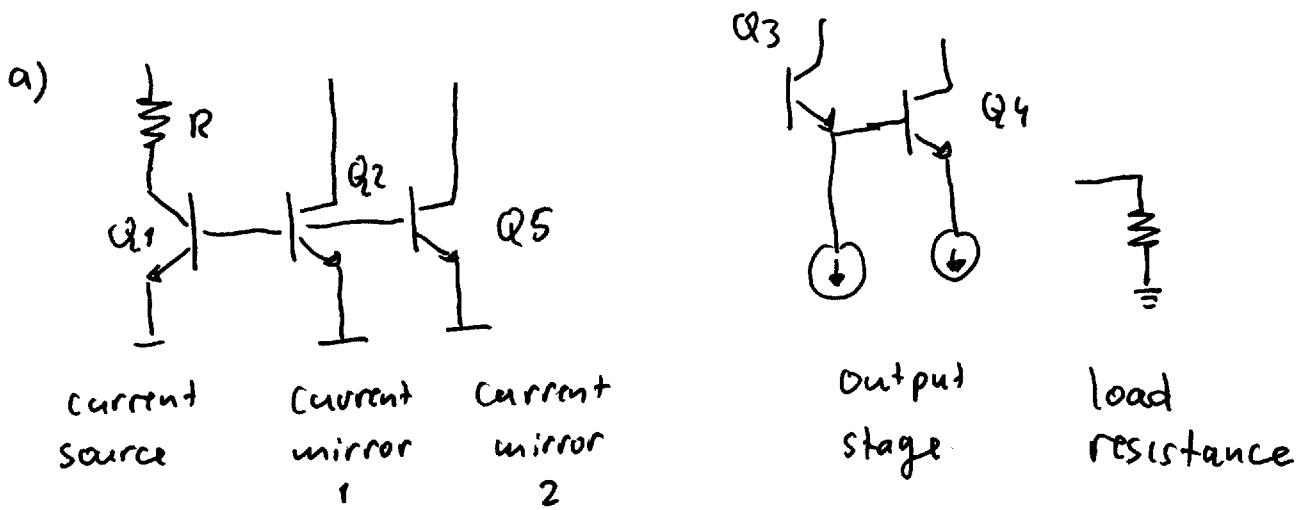

$$I_{E1} \text{ (at } \otimes \text{)} : I_S = \frac{\beta}{\beta+1} + \frac{12}{\beta+1} = \frac{\beta+12}{\beta+1} \times I_{E1} \quad \left(I_{E1} = \frac{\beta+1}{\beta+12} I_S \right)$$

$$I_{C5} = \frac{10\beta}{\beta+1} I_{E1} = \frac{10\beta}{\beta+1} \times \frac{\beta+1}{\beta+12} I_S = 10 \frac{\beta}{\beta+12} I_S$$

$$I_{C2} = \frac{\beta}{\beta+1} I_{E1} = \frac{\beta}{\beta+1} \cdot \frac{\beta+1}{\beta+12} I_S = \frac{\beta}{\beta+12} I_S$$

$$I_{C3} = \frac{\beta}{\beta+1} I_{C2} = \frac{\beta^2}{(\beta+1)(\beta+12)} I_S$$


$$I_{C4} = \frac{\beta}{\beta+1} I_{C5} = 10 \frac{\beta^2}{(\beta+1)(\beta+12)} I_S$$

c) Class A (360° phase is passed)

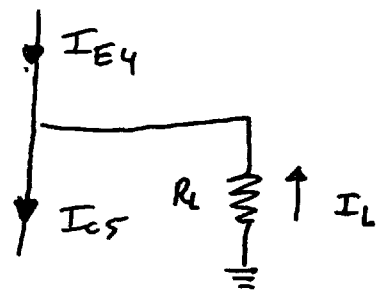d) - It is limited by V_{CC}

- It is limited by I_{CS} . Q4 cannot deliver negative current. Minimum is 0

For negative output voltage we have the situation here on the left




Ideally, $I_{CS} = \frac{V_{CC}}{R_L}$

But, $I_{CS} = 10 I_S$

$I_S = \frac{V_{CC} - V_{EE} - 0.7V}{R}$

$I_S \approx \frac{2 V_{CC}}{R}$

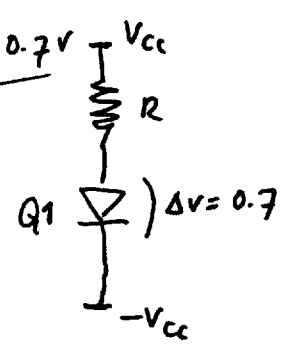$I_{CS} \approx \frac{20 V_{CC}}{R} = \text{ideally } \frac{V_{CC}}{R_L}$



$\Rightarrow R = 20 R_L$ ideally

e) (Equal to example in lecture notes)

We assume maximum output, with R as above

$V_o = V_{CC} \sin \omega t$

$P_L(t) = V_o(t) \cdot \frac{V_o(t)}{R_L} = \frac{V_{CC}^2 \sin^2 \omega t}{R_L}$

$\bar{P}_L = \frac{1}{T} \int_0^T P_L(t) dt = \frac{1}{T} \int_0^T \frac{V_{CC}^2 \sin^2 \omega t}{R_L} dt = \frac{V_{CC}^2}{2R_L}$

power supplied by $-V_{EE}$ (only Q5) :


$$P_{EE} = V_{EE} \times I_{ES} = V_{CC} \times \frac{V_{CC}}{R_L} = \frac{V_{CC}^2}{R_L}$$

power supplied by $+V_{CC}$ (only Q4)

$$P_{CC}(t) = V_{CC}(t) \times I_{C4}(t) =$$

$$(I_{C4} = I_L + I_{CS})$$
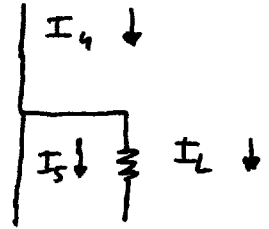
$$= V_{CC} \times \left(\frac{V_{CC} \sin \omega t}{R_L} + \frac{V_{CC}}{R_L} \right)$$



$$\begin{aligned} \bar{P}_{CC} &= \int_0^T P_{CC}(t) dt = \frac{1}{T} \int_0^T \left[\frac{V_{CC}^2 \sin^2 \omega t}{R_L} + \frac{V_{CC}^2}{R_L} \right] dt \\ &= \frac{V_{CC}^2}{R_L} \end{aligned}$$

$$\text{total power } \bar{P}_S = \bar{P}_{CC} + \bar{P}_{EE} = \frac{2V_{CC}^2}{R_L}$$

$$\text{Efficiency } \eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{V_{CC}^2 / 2R_L}{2V_{CC}^2 / R_L} = \frac{1}{4} = 25\%$$


f) $R_L = 10 \Omega$, $V_{CC} = 15V$

$$\bar{P}_L = \frac{(15V)^2}{2 \times 10\Omega} = 11.25W$$

$$\bar{P}_S = 45W$$

$$\bar{P}_{CC} = 22.5W, \quad \bar{P}_{EE} = 22.5W$$

Q5

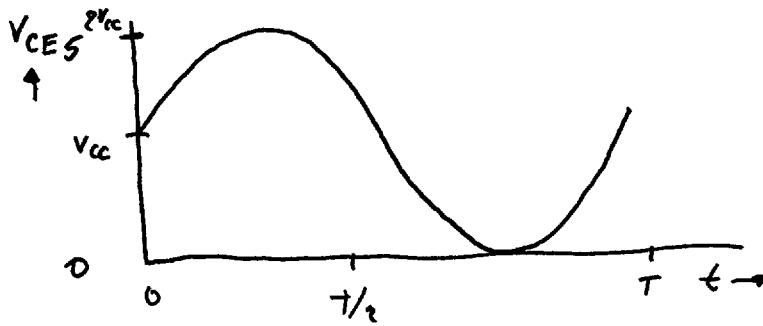


$$P_{Q5} = V_{CE5}(t) \times I_{C5}(t)$$

$$= V_{CC} (1 + \sin \omega t) \times \frac{V_{CC}}{R_L}$$

$$\bar{P}_{Q5} = \frac{1}{T} \int_0^T \frac{V_{CC}^2}{R_L} (1 + \sin \omega t) dt = \frac{V_{CC}^2}{R_L} = \frac{(15V)^2}{10\Omega} = 22.5W$$

Q4

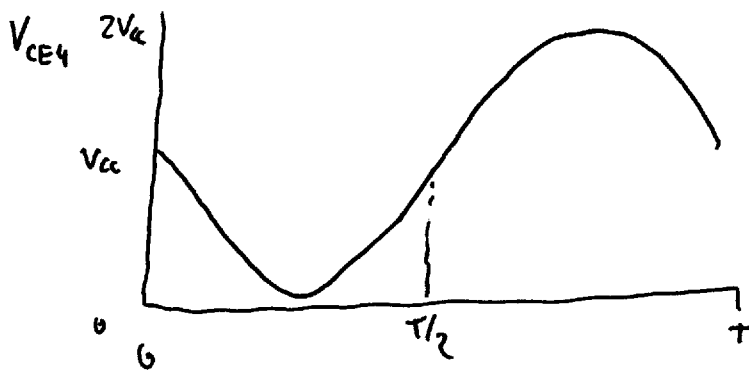

Should give

$$45W - 22.5W - 11.25W = 11.25W$$

$$P_{Q4}(t) = V_{CE4}(t) \times I_{C4}(t)$$

$$= V_{CC} (1 - \sin \omega t) \times \left(\frac{V_{CC} \sin \omega t}{R_L} + \frac{V_{CC}}{R_L} \right)$$

$$= \frac{V_{CC}^2}{R_L} (1 - \sin \omega t) (1 + \sin \omega t)$$

$$= \frac{V_{CC}^2}{R_L} (1 - 2 \sin \omega t + \sin^2 \omega t)$$

$$\bar{P}_{Q4} = \frac{1}{T} \int_0^T P_{Q4}(t) dt = \frac{V_{CC}^2}{R_L} \left(1 - \frac{1}{2} \right) = \frac{V_{CC}^2}{2R_L} = 11.25W$$

g) Q4: $T_4 = 25^\circ\text{C} + \theta \times \bar{P}_{Q4}$
 $= 25^\circ\text{C} + 20^\circ\text{C/W} \times 11.25 \text{ W} = 250^\circ\text{C}$
burn!

Q5: $T_5 = 25^\circ\text{C} + \theta \times \bar{P}_{Q5}$
 $= 25^\circ\text{C} + 20^\circ\text{C/W} \times 22.5 \text{ W} = 475^\circ\text{C}$
burn!

